

Study of the characteristics of an NPN Bipolar Junction Transistor

PH3204 - Electronics Laboratory

Debayan Sarkar

22MS002

Group B-10

February 16, 2025

1 Aim

In this experiment we study the characteristics of an n-p-n bipolar junction transistor (BJT).

2 Theory and Experimental Setup

2.1 NPN Bipolar Junction Transistor

Bipolar Junction Transistors (BJTs) are utilized in circuits as switches and for signal amplification. BJT comes in two varieties: npn and pnp. The npn BJT will be the subject of this experiment. The emitter, base, and collector are the three semiconductor layers that make up the npn BJT. The base is lightly doped, the collector is moderately doped, and the emitter is strongly doped. The emitter-base junction and the collector-base junction are the two junctions found in the BJT. We will examine the BJT in the Common Emitter (CE) configuration, while it can be utilized in a variety of other setups. In this setup, the base receives the input, while the collector receives the output.

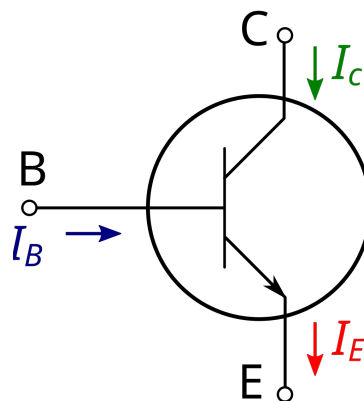


Figure 1: NPN Bipolar Junction Transistor (Source: The Internet)

Both the input and the output share the emitter. The plot of the base current (I_b) against the base-emitter voltage (V_{BE}) for a fixed collector voltage (V_{CC}) is the BJT's input characteristics. The plot of the collector current (I_c) against the collector-emitter voltage (V_{CE}) for a fixed base current (I_b) represents the BJT's output characteristics.

In this experiment We also examine the BJT's current gain. The collector base junction is reverse biased and the base emitter junction is forward biased when the BJT is utilized as an amplifier. The electrons move from the emitter to the base in a forward bias and from the base to the collector in a reverse bias.

The base current I_b is created by a tiny bit of recombination in the base area. The collector current I_c , which is determined by the following formula, is nearly equal to I_E :

$$I_c = \alpha I_E$$

with $\alpha \approx 1$. The current gain of the BJT is given by the formula:

$$\beta = \frac{I_c}{I_b}$$

where $\beta = \frac{\alpha}{1 - \alpha}$ which could be quite large.

2.2 Experimental Setup

The circuit for this experiment was prepared on a breadboard. Below is the Circuit Diagram for the setup used in this experiment.

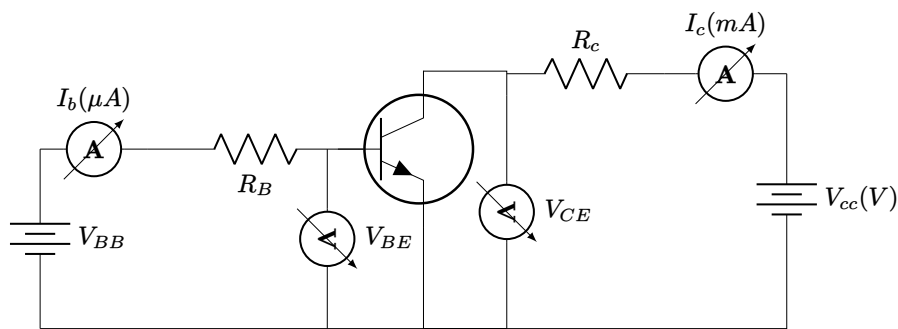


Figure 2: Circuit diagram of an npn BJT in the common emitter configuration

3 Data and Analysis

The Data tables for both parts of this experiment can be found in the supplementary section.

3.1 Input Characteristics

In this part of the experiment, we studied the input characteristics of the given transistor. We fixed the collector voltage (V_{CC}) and then varied the base voltage (V_{BB}) and measured the base current (I_b). We had set $R_B = 1k\Omega$. We took datasets for $V_{CC} = 2V, 3V, 4V$

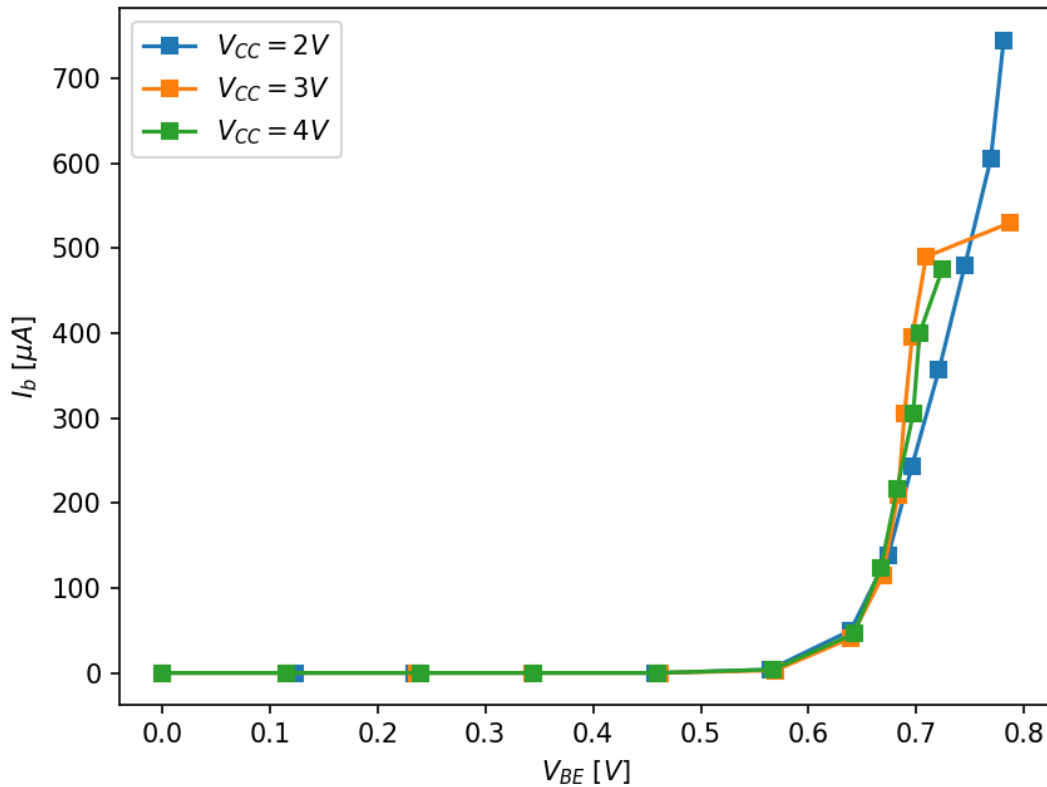


Figure 3: Input Characteristics of the given NPN BJT

The shape of the curves matches the theoretical predictions. We expected the 2V line to be to the left of the other two, however we observed the opposite.

3.2 Output Characteristics

In this part of the experiment we studied the output characteristics of the given transistor. We fixed the base current (I_b), and varied the collector-emitter voltage (V_{CE}) and measured the collector current (I_c). We took three datasets for $I_b = 10, 20, 30\mu A$. We had set $R_B = 220\Omega$ and $R_c = 1k\Omega$.

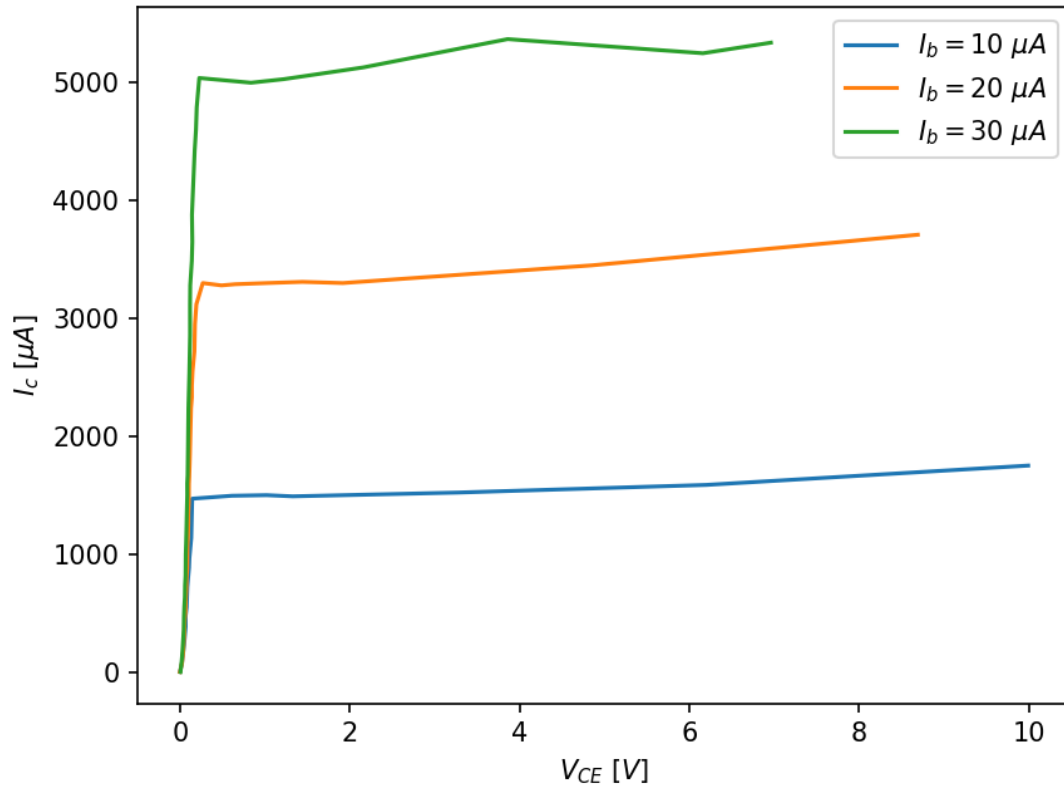


Figure 4: Output Characteristics of the given NPN BJT

As expected, the $I_b = 30\mu A$ curve is at the top, and the $I_b = 10\mu A$ curve is at the bottom. Also, the shape of the curves matches the theoretical predictions.

3.3 Current Gain of the BJT

We know that the current gain of the BJT is given by the formula:

$$\beta = \frac{I_c}{I_b}$$

To get the Current gain, we plotted I_c vs I_b as obtained in the input characteristics part of the experiment. Then, we took a linear fit of the data, to get the following values of β at different V_{BE} 's:

$$\beta_{2V} = 131.28 \pm 0.31$$

$$\beta_{3V} = 201.77 \pm 3.52$$

$$\beta_{4V} = 205.31 \pm 3.64$$

As expected from the theory, β is of the order of 10^2 , which is quite large.

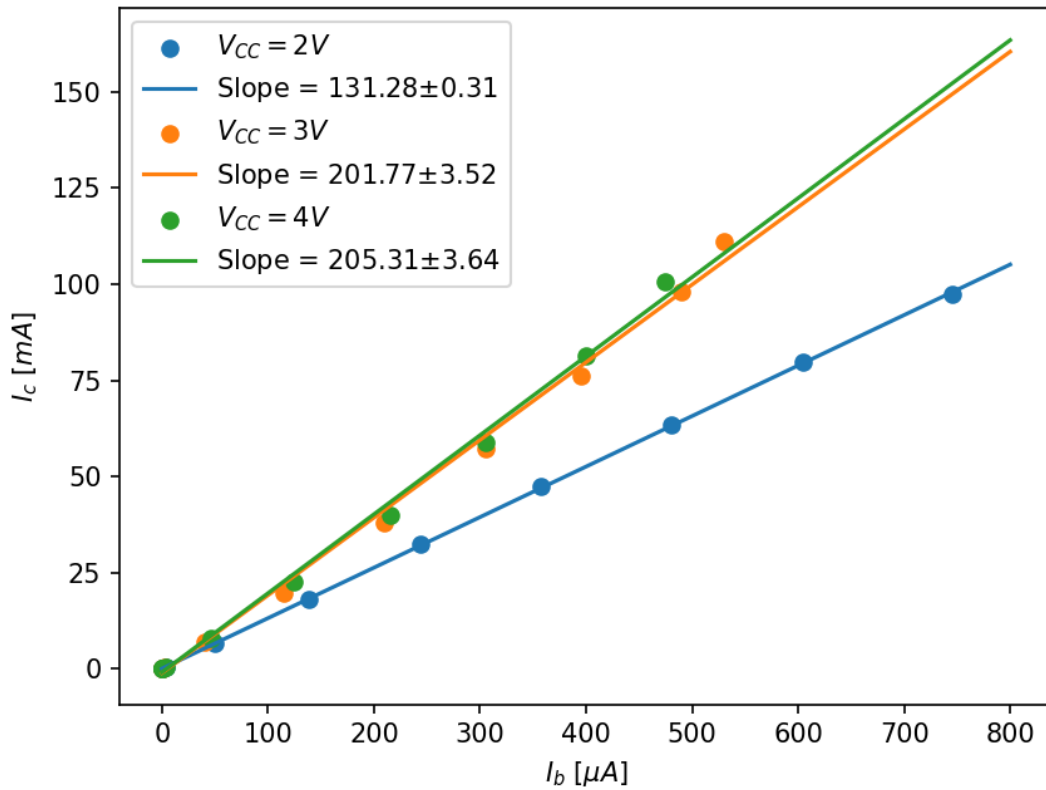


Figure 5: Current Gain of the given NPN BJT

4 Conclusion

In conclusion, in this experiment we used the given BJT in Common Emmitter mode and collected the input and output characteristics of the given NPN BJT, and we also measured the current gain of the transistor.

5 Sources Of Error

1. The power source voltage was fluctuating, which could cause inaccuracies in the measurements.
2. While collecting the output characteristics, the I_b readings kept fluctuating, with a deviation of $\pm 3\mu A$
3. Loose Contacts between the Breadboard and the components, could lead to fluctuations in measurements.
4. The multimeters are not ideal ammeters or voltmeters, hence the reading given by them isnt exact. Inaccucies due to the finite internal resistance of these devices also leads to some errors in the measurements.

6 Supplementary

V_BB	V_BE	I_b (micro A)	I_c(mA)	V_CC	V_CE
0	0	0	0	2	2
0.1	0.1232	0	0	2	2
0.2	0.234	0	0	2	2
0.4	0.458	0	0.007	2	2
0.5	0.564	4	0.4	2	2
0.6	0.639	50	6.62	2	2
0.7	0.674	139	18.23	2	2
0.8	0.696	244	32.3	2	2
0.9	0.721	357	47.4	2	2
1	0.745	480	63.4	2	2
1.1	0.769	605	79.6	2	2
1.2	0.781	745	97.3	2	2

Table 1: BJT Input Characteristics at $V_{CC} = 2V$

V_BB	V_BE	I_b (micro A)	I_c(mA)	V_CC	V_CE
0	0	0	0	3	3
0.1	0.1156	0	0	3	3
0.2	0.236	0	0	3	3
0.3	0.343	0	0	3	3
0.4	0.462	0	6.00E-03	3	3
0.5	0.569	3	4.88E-01	3	3
0.6	0.639	41	6.95	3	3
0.7	0.669	115	19.86	3	3
0.8	0.683	210	38.1	3	3
0.9	0.689	305	57.1	3	3
1	0.696	395	76.3	3	3
1.1	0.709	490	98.1	3	3
1.2	0.787	530	111.2	3	3

Table 2: BJT Input Characteristics at $V_{CC} = 3V$

V_BB	V_BE	I_b (micro A)	I_c(mA)	V_CC	V_CE
0	0	0	0	4	4
0.1	0.115	0	0	4	4
0.2	0.24	0	0	4	4
0.3	0.345	0	0	4	4
0.4	0.46	0	0.01	4	4
0.5	0.567	4	0.556	4	4
0.6	0.642	46	8.03	4	4
0.7	0.667	124	22.6	4	4
0.8	0.682	216	40	4	4
0.9	0.697	305	58.8	4	4
1	0.703	400	81.4	4	4
1.1	0.724	475	100.6	4	4

Table 3: BJT Input Characteristics at $V_{CC} = 4V$

V_BB	I_b (micro A)	I_c(micro A)	V_CC	V_CE
0.44	10	0	0	0
0.46	10	70	0.1	0.0233
0.47	10	151	0.2	0.0367
0.47	10	226	0.3	0.0489
0.48	10	305	0.4	0.0584
0.5	10	385	0.5	0.0682
0.49	10	477	0.6	0.0677
0.49	10	549	0.7	0.0798
0.49	10	635	0.8	0.0837
0.49	10	720	0.89	0.0878
0.49	10	805	1	0.0978
0.5	10	882	1.1	0.1075
0.5	10	968	1.2	0.1122
0.5	10	1137	1.4	0.1335
0.51	10	1470	1.8	0.1444
0.51	10	1495	2.3	0.611
0.51	10	1.50E+03	2.7	1.021
0.51	10	1.49E+03	3	1.328
0.5	10	1522	4.98	3.27
0.5	10	1587	8	6.2
0.5	10	1751	11.97	9.99

Table 4: BJT Output Characteristics at $I_b = 10 \mu A$

V_BB	I_b (micro A)	I_c(micro A)	V_CC	V_CE
0.47	20	0	0	0
0.49	20	72	0.1	0.0243
0.5	20	173	0.22	0.0393
0.5	20	251	0.31	0.0452
0.51	20	333	0.4	0.052
0.51	20	440	0.52	0.0562
0.52	20	508	0.6	0.0653
0.52	20	602	0.7	0.0686
0.52	20	696	0.8	0.0749
0.53	20	788	0.9	0.0781
0.53	20	878	1	0.0862
0.53	20	974	1.09	0.0876
0.53	20	1067	1.19	0.0894
0.53	20	1162	1.3	0.0955
0.53	20	1258	1.4	0.0997
0.53	20	1349	1.49	0.1004
0.53	20	1437	1.59	0.1051
0.54	20	1593	1.74	0.1063
0.54	20	1657	1.82	0.1102
0.54	20	1761	1.92	0.1146
0.54	20	1846	2	0.1179
0.54	20	1955	2.11	0.1214
0.54	20	2240	2.22	0.131
0.54	20	2330	2.32	0.141
0.54	20	2430	2.41	0.141
0.54	20	2550	2.52	0.149
0.54	20	2720	2.7	0.171
0.54	20	2950	2.9	0.177
0.54	20	3120	3.08	0.194
0.54	20	3300	3.33	0.269
0.54	20	3280	3.53	0.489
0.54	20	3290	3.7	0.65
0.54	20	3300	4.07	1.023
0.54	20	3310	4.5	1.443
0.54	20	3300	5	1.92
0.54	20	3450	8.05	4.85
0.54	20	3710	12.11	8.69

Table 5: BJT Output Characteristics at $I_b = 20 \mu A$

V_BB	I_b (micro A)	I_c(micro A)	V_CC	V_CE
0.47	30	0	0	0.0069
0.48	30	87	0.1	0.0202
0.49	30	167	0.2	0.0295
0.49	30	274	0.31	0.0382
0.5	30	358	0.4	0.0451
0.51	30	459	0.51	0.0472
0.51	30	551	0.61	0.0516
0.51	30	634	0.7	0.0581
0.51	30	737	0.8	0.0603
0.51	30	818	0.89	0.0662
0.51	30	904	0.99	0.0675
0.52	30	997	1.08	0.0686
0.52	30	1108	1.2	0.0735
0.52	30	1209	1.3	0.0771
0.52	30	1319	1.42	0.0803
0.53	30	1358	1.47	0.0815
0.53	30	1499	1.61	0.0865
0.53	30	1599	1.71	0.0861
0.53	30	1669	1.78	0.0911
0.53	30	1894	2.02	0.0951
0.53	30	2240	2.19	0.1002
0.54	30	2540	2.48	0.1112
0.54	30	2860	2.8	0.1197
0.54	30	3110	3.04	0.1191
0.54	30	3280	3.21	0.1213
0.54	30	3490	3.42	0.1404
0.54	30	3650	3.62	0.1464
0.54	30	3880	3.79	0.1422
0.55	30	4180	4.09	0.1595
0.55	30	4430	4.33	0.1743
0.55	30	4600	4.5	0.189
0.55	30	4790	4.71	0.198
0.55	30	5040	4.94	0.228
0.55	30	5000	5.53	0.837
0.55	30	5030	5.97	1.221
0.55	30	5130	7.02	2.16
0.55	30	5370	8.96	3.86
0.55	30	5250	11.13	6.16
0.55	30	5340	11.98	6.96

Table 6: BJT Output Characteristics at $I_b = 30 \mu A$